

Physics 401

Pulses in Transmission Lines

(week of February 14th)

- Comment on the Lab-Quiz
- Pulses in Transmission Lines




Quiz → Lab-Discussion

- Don't work on it at home!
- TAs will distribute the lab-discussion sheets in class.
 - ➔ collaborate with other students + TA in answering the questions!




Comments:

- RLC pre-lab

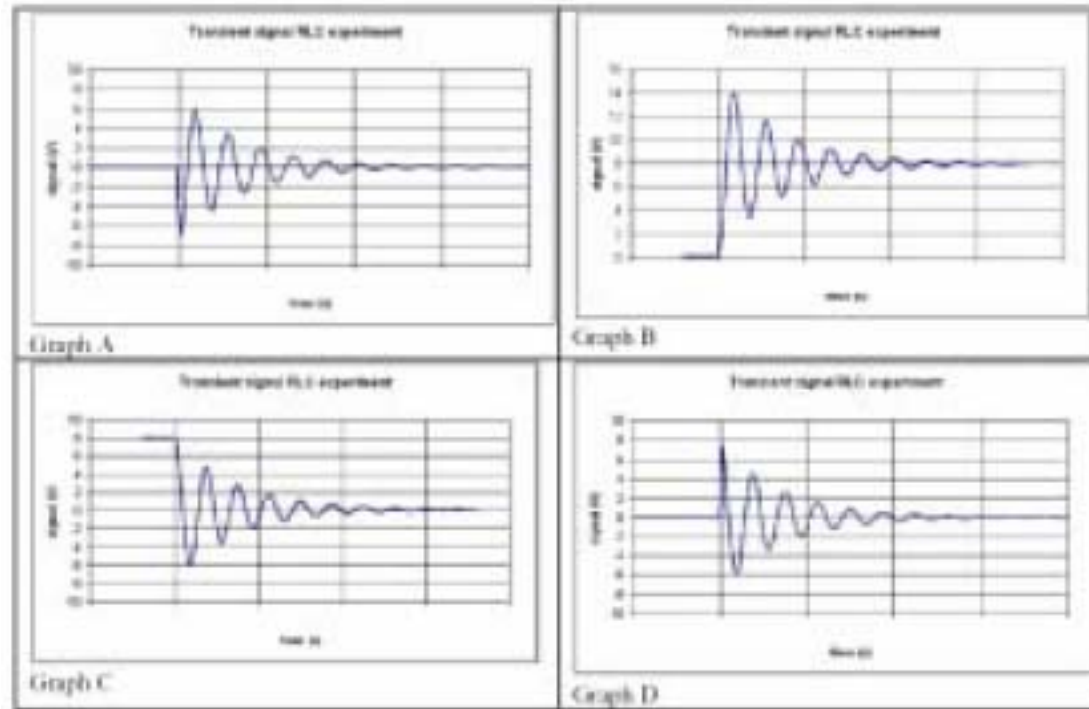


- Counting Experiment: How to treat the error on the background.


Pulses in Transmission Lines

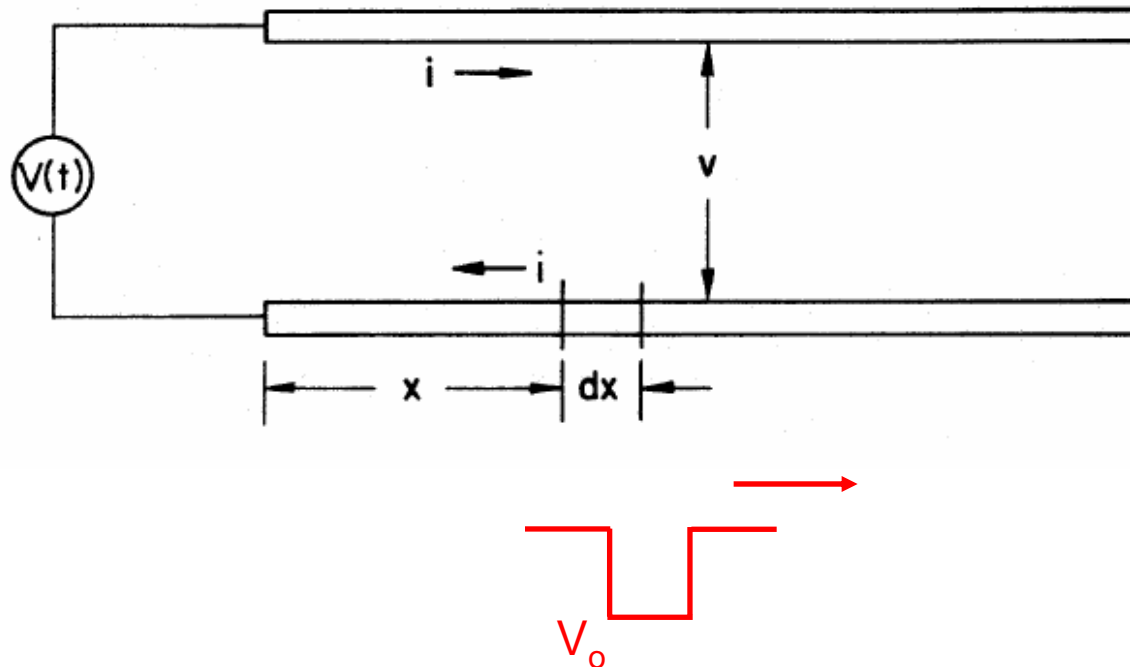


Experimental Setup I

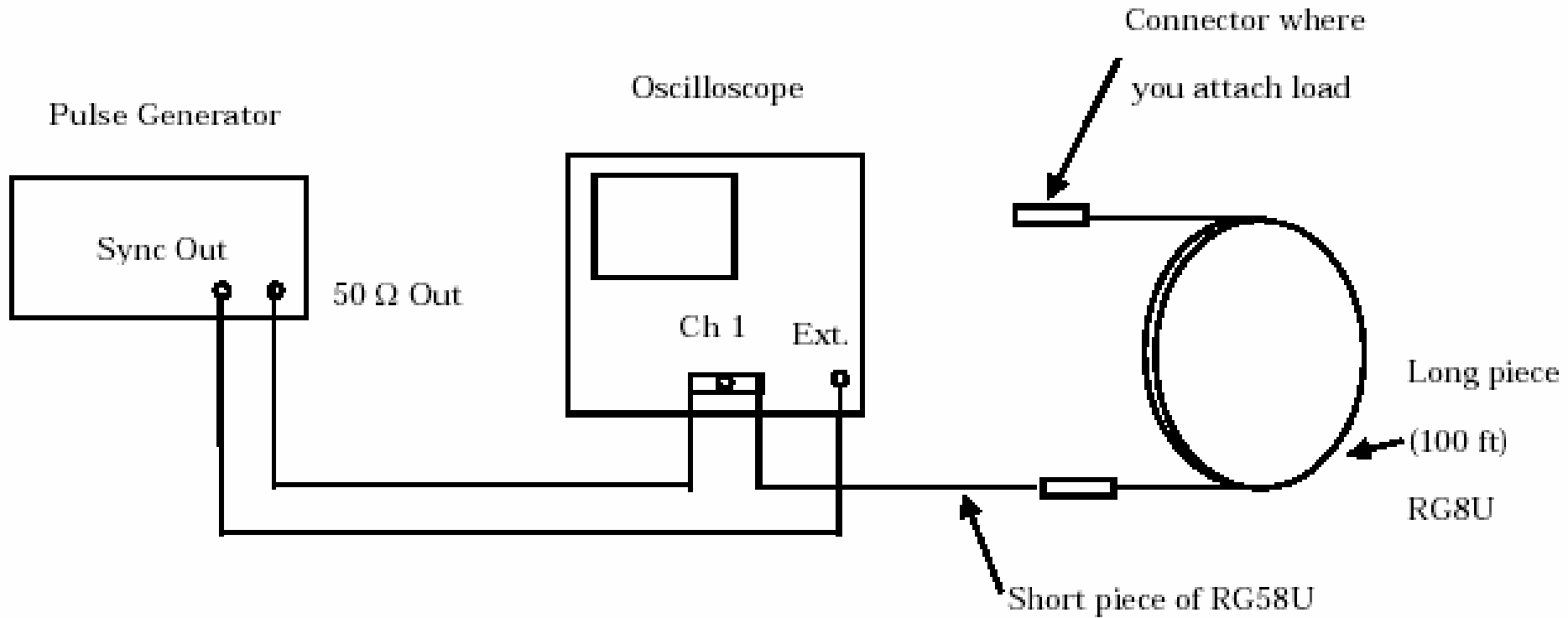

Experimental Setup II

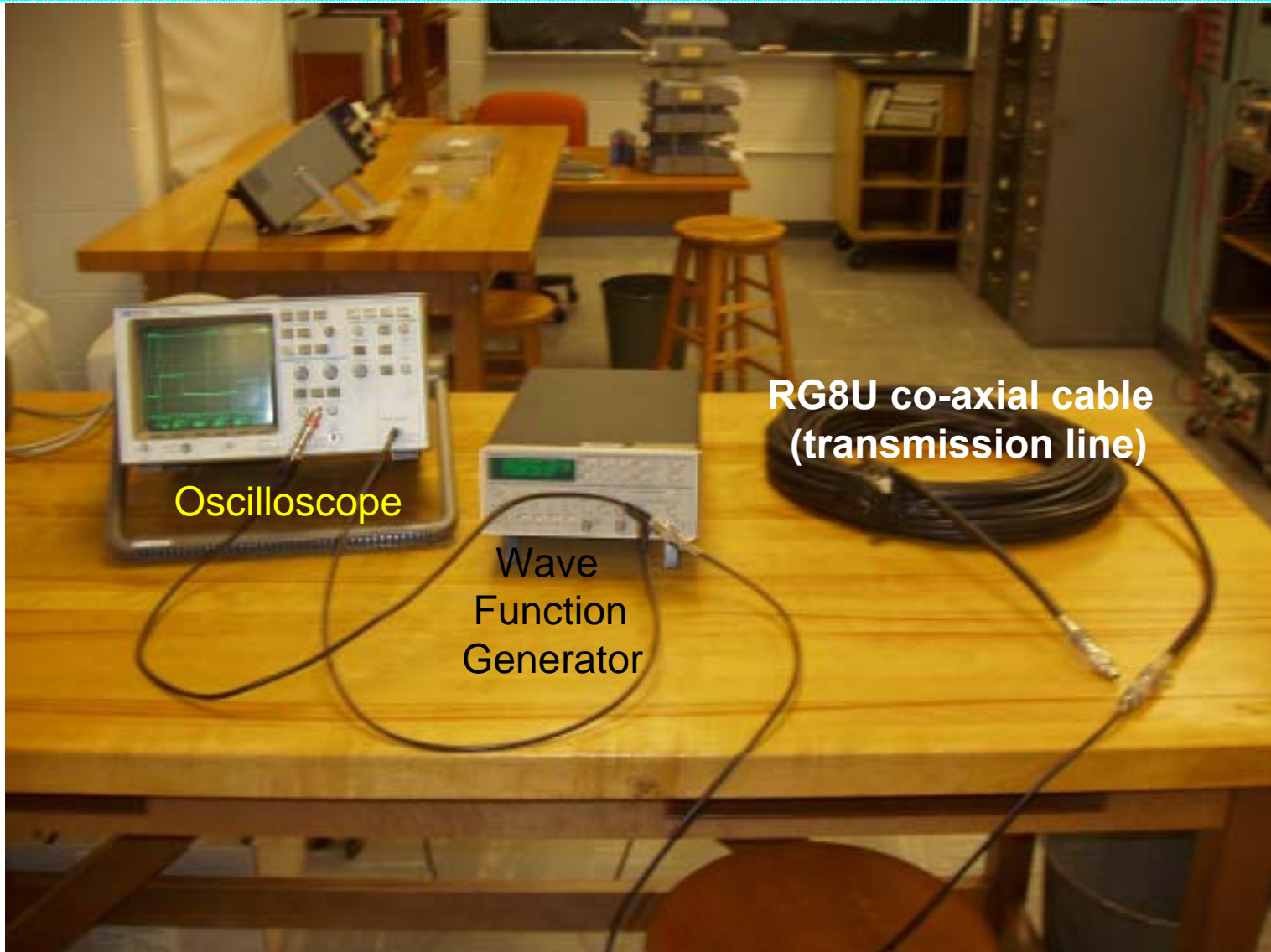


Co-axial Cables (eg. RG8U)

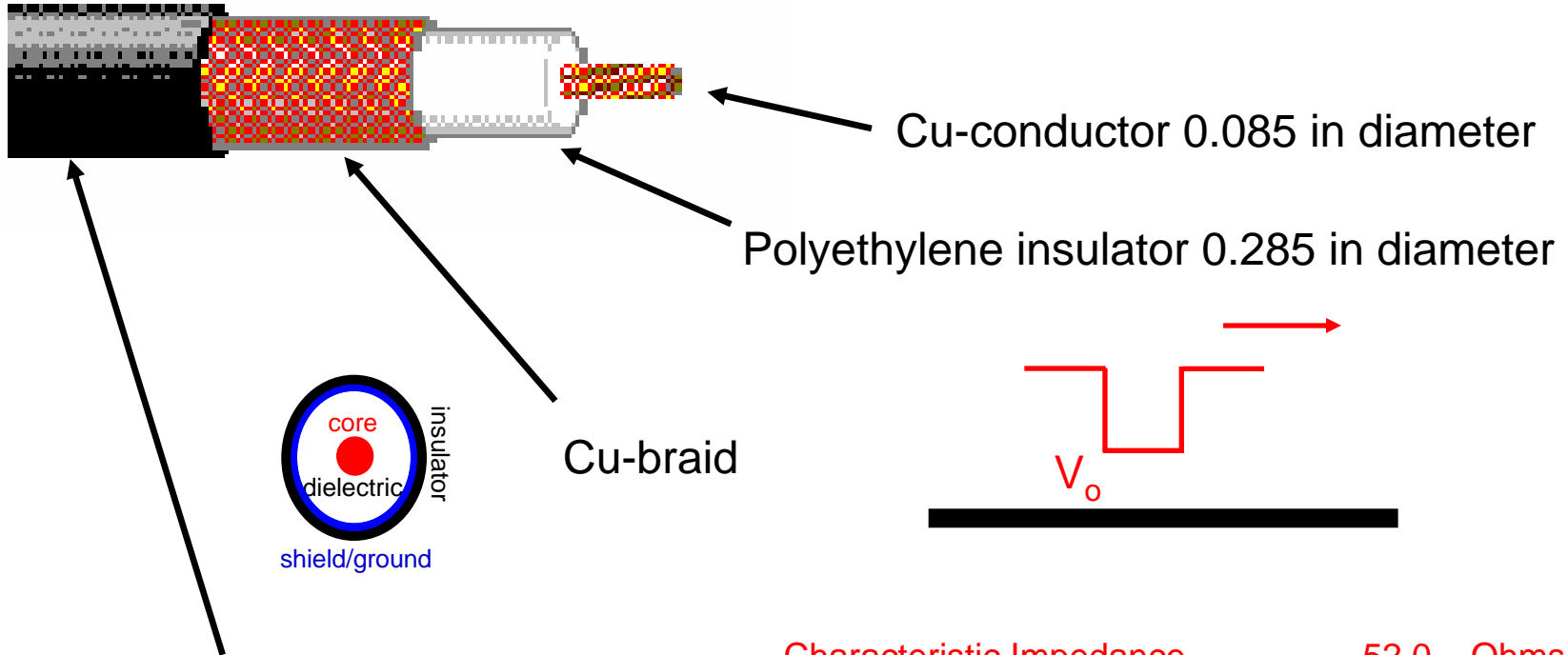


PVC outer jacket 0.405 in diameter

Characteristic Impedance	52.0	Ohms
Inductance	0.079	$\mu\text{H}/\text{ft}$
Capacitance Conductor to Shield	28.5	pF/ft
Velocity of Propagation	0.66	c
Delay	1.54	ns/ft

Signal Propagation

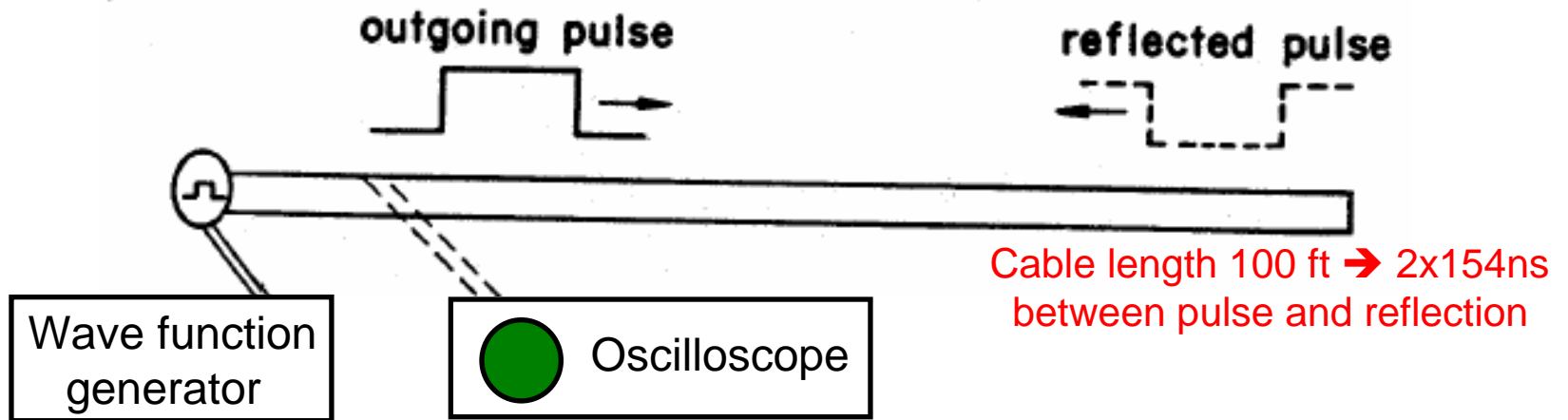

open line

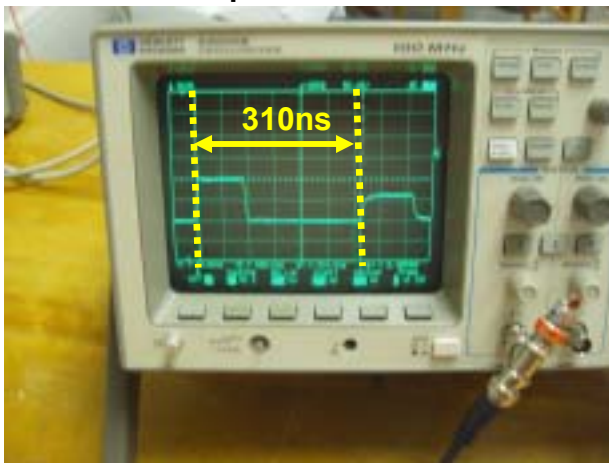


shorted line



The Wave Equation

$$di = -(Cdx) \frac{dV}{dt},$$

C = capacitance per unit length

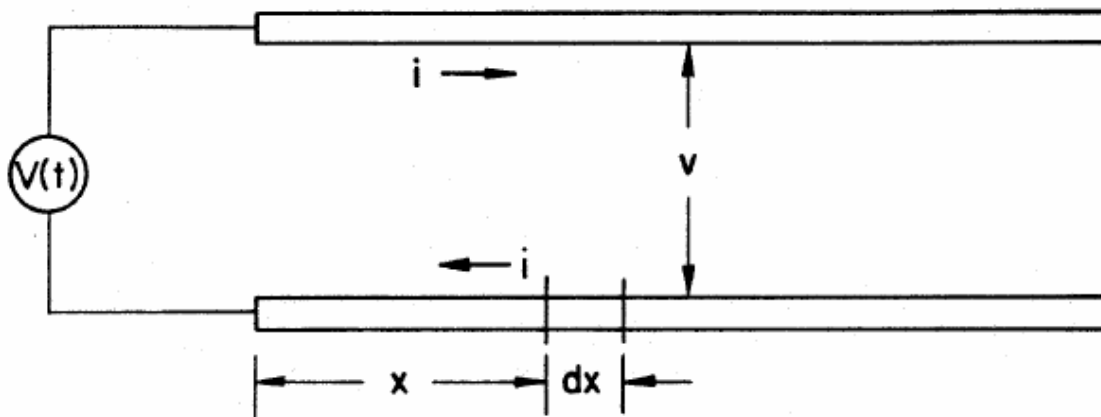

$$dV = -(Ldx) \frac{di}{dt},$$

L = inductance per unit length


$$\frac{\partial i}{\partial x} = -C \frac{\partial V}{\partial t}$$

$$\frac{\partial V}{\partial x} = -L \frac{\partial i}{\partial t}$$




The Wave Equation
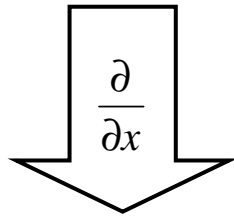
$$\frac{\partial V}{\partial x} = -L \frac{\partial i}{\partial t}$$



$$\frac{\partial^2 V}{\partial x^2} = -L \frac{\partial^2 i}{\partial x \partial t}$$
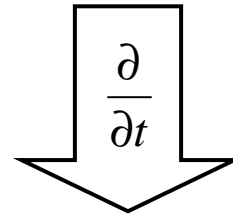
$$\frac{\partial i}{\partial x} = -C \frac{\partial V}{\partial t}$$



$$\frac{\partial^2 i}{\partial t \partial x} = -C \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2} \quad \frac{\partial^2 i}{\partial x^2} = LC \frac{\partial^2 i}{\partial t^2}$$

Voltage and Current Waves

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 i}{\partial x^2} = LC \frac{\partial^2 i}{\partial t^2}$$

$$V(x, t) = V_0 \sin \omega \left(t - \frac{x}{v} \right), \quad v = \frac{1}{\sqrt{LC}}$$


$$i(x, t) = i_0 \sin \omega \left(t - \frac{x}{v} \right), \quad v = \frac{1}{\sqrt{LC}}$$

$$V(x, t) = \sqrt{\frac{L}{C}} i(x, t) = Z_k i(x, t)$$

Z_k : characteristic Impedance



Reflection of Pulses at Resistive Loads

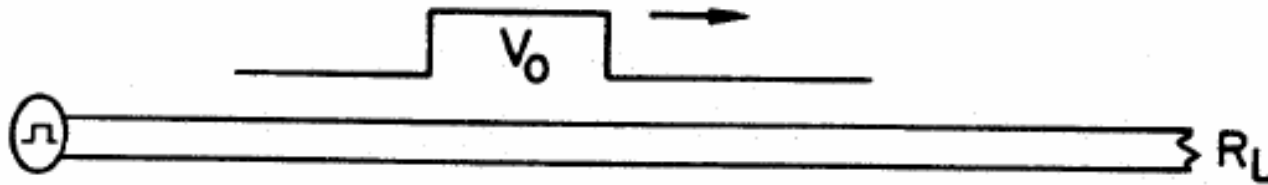

$$R_L = \frac{V}{i} = \frac{V_r + V_i}{V_i - V_r} Z_k$$

$$\Rightarrow V_r = \frac{R_L - Z_k}{R_L + Z_k} V_i$$


$$\Rightarrow V_r = V_i = V_0, \quad \text{if } R_L = \infty$$

Termination resistor disconnected


$$\Rightarrow V_r = -V_i = -V_0, \quad \text{if } R_L = 0$$

Termination resistor shorted


Incoming vs Reflected Wave

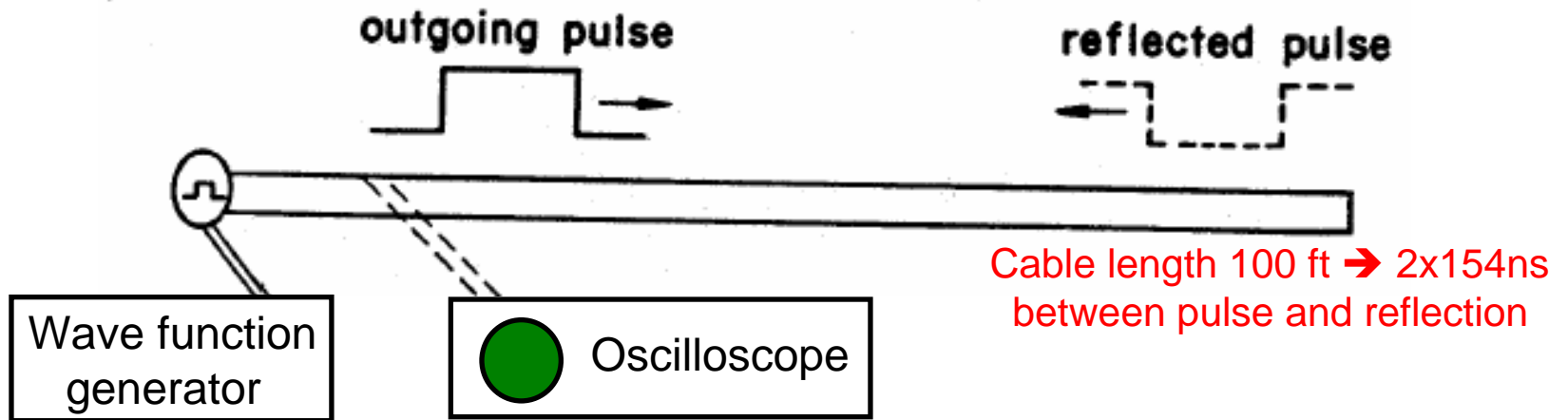

open line

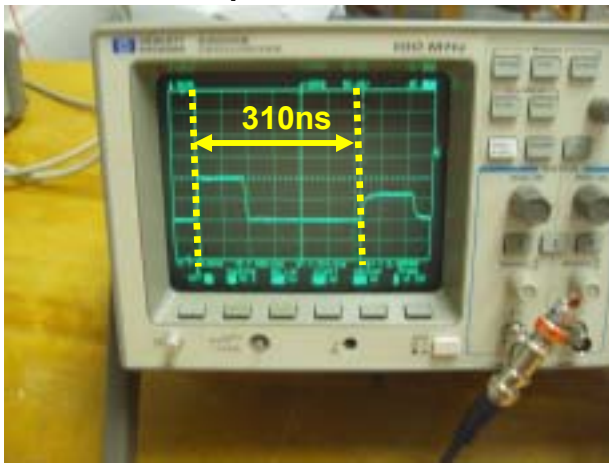

shorted line

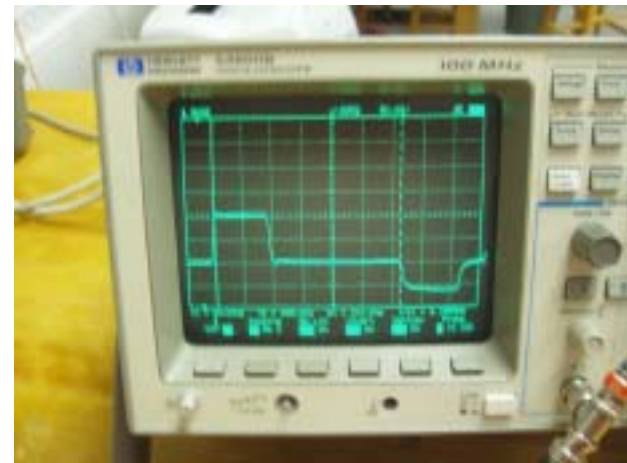


Error Propagation

Derive f from measured quantities
quantities $x_i \pm \Delta x_i$

$$f = f(x_1, \dots, x_n)$$

Error Δf on f :
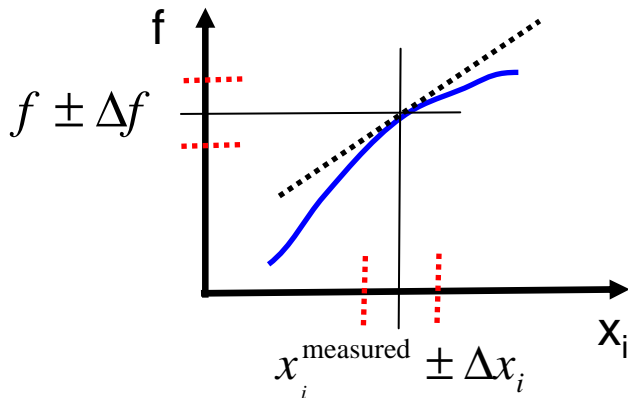
$$\Delta f(x_i, \Delta x_i) = \sqrt{\sum_{i=1}^n \left[\frac{\partial f}{\partial x_i} \right]^2 \cdot \Delta x_i^2}$$



Example: Frequency in LC circuit

Derive frequency f
from measured inductance

$L \pm \Delta L$ and capacitance $C \pm \Delta C$

$$f(L, C) = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 503.6 \pm 56.3 \text{ Hz},$$

$$L = 10 \pm 1 \text{ mH}, \quad C = 10 \pm 2 \mu\text{F}$$

Error Δf on f :

$$\Delta f(L, C, \Delta L, \Delta C) = \sqrt{\left[\frac{\partial f}{\partial L}\right]^2 \cdot \Delta L^2 + \left[\frac{\partial f}{\partial C}\right]^2 \Delta C^2}$$

$$\frac{\partial f}{\partial L} = \frac{-1}{4\pi} C^{-\frac{1}{2}} L^{-\frac{3}{2}}$$

$$\frac{\partial f}{\partial C} = \frac{-1}{4\pi} L^{-\frac{1}{2}} C^{-\frac{3}{2}}$$

